

Digital Design Lab 8

Name:Dhruv

Roll Number: B20EE016

Task 1: 8 bit MLS counter using LFSR

Code:


```
`timescale 1ns / 1ps

module MLSCounter(clk, LFSR);
input clk;
output reg [7:0] LFSR = 42;
wire w1 = LFSR[3];
wire w2 = LFSR[2];
wire w3 = LFSR[1];
wire w4 = LFSR[7];
always@(posedge clk)
begin
    LFSR[7:1] <= LFSR[6:0];
    LFSR[0] <= LFSR[3]^LFSR[4]^LFSR[5]^LFSR[7];
end
endmodule
```

Test Bench:


```
module MLSCountertest;
reg clk;
wire [7:0] LFSR;
MLSCounter mls(clk, LFSR);
initial begin
    clk = 0;
end
always #10 clk = ~clk;
initial #180 $finish;
endmodule
```

Waveform:

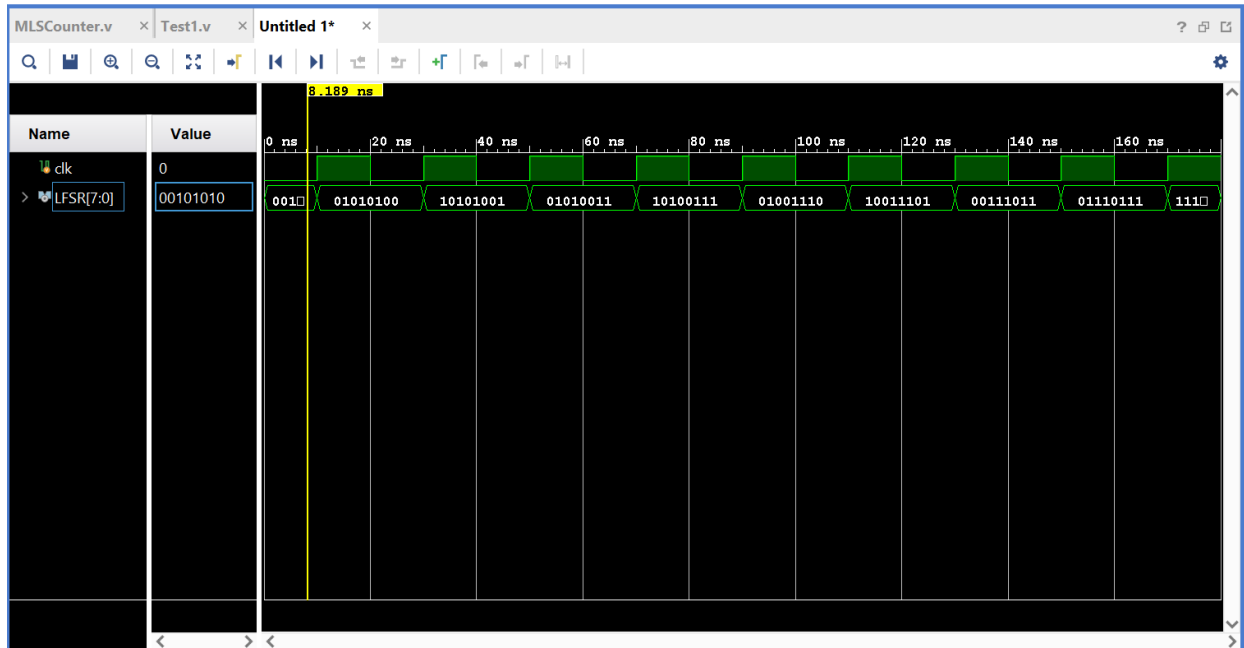

Task 2: 2's complement of a running bitstream using

a) Mealy Machine

 

Code:

```
module melay_machine(clk, reset, a, out, ps, ns);
  input a;
  input clk, reset;
```

```

output reg out;
output reg ps, ns;
parameter s0 = 1'b0;
parameter s1 = 1'b1;
always@(posedge clk, negedge reset)
begin
    if(!reset)
        ps <= s0;
    else
        ps <= ns;
end
always@(ps, a)
begin
    case(ps)
    s0: if(a)
        begin
            ns <= s1;
            out <= 1;
        end
    else
        begin
            ns<=s0;
            out<=0;
        end
    s1: if(a)
        begin
            out <= 0;
            ns <= s1;
        end
    else
        begin
            out <= 1;
            ns <= s1;
        end
    endcase
end
endmodule

```

Test Bench:

```

module test_melay2_complement;
reg clk, reset;
reg a;
wire out;
wire ps, ns;
melay_machine mc(clk, reset, a, out, ps, ns);
always #5 clk = ~clk;
initial
begin

```


```

clk = 0;
reset = 0;
a = 1;
#10 reset = 1;
#10 a = 0;
#10 a = 1;
#10 a = 1;
#10 a = 0;
#10 a = 1;
#10 a = 0;
#10 a = 1;
#10 a = 1;
#10 a = 1;
end


initial #110 $finish;
endmodule

```

Waveform:

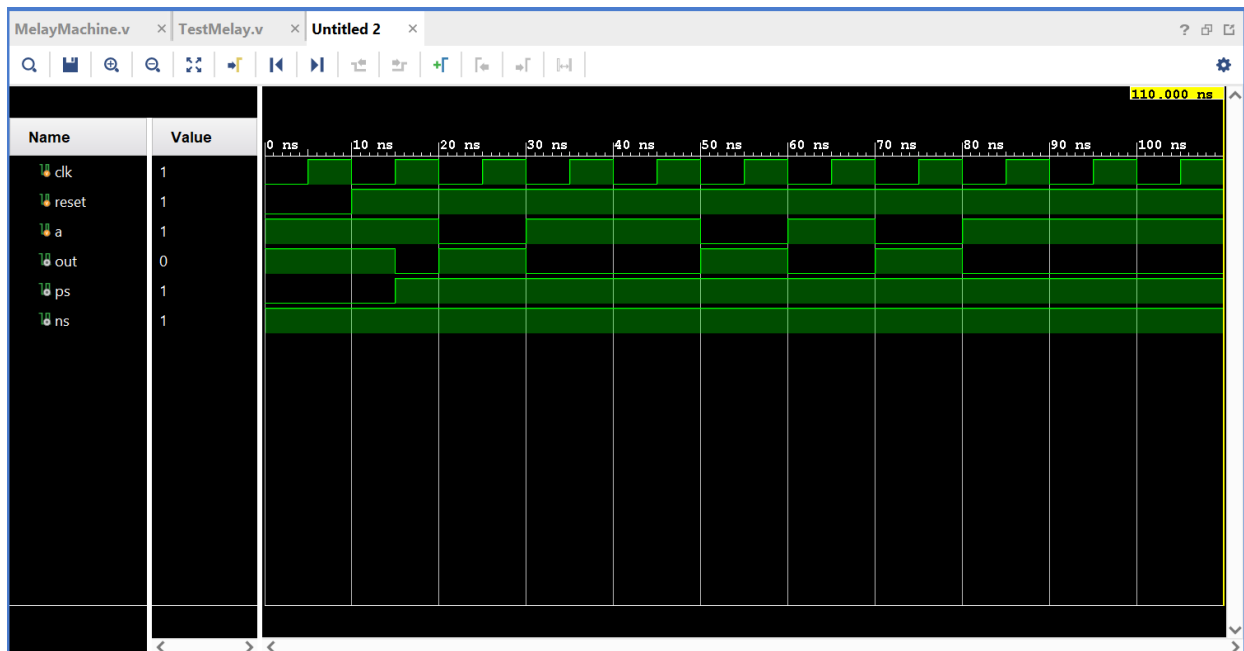

b) Moore Machine

 

Code:

```

module moore_machine(clk, reset, a, out, state);
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
integer i;
input clk, reset, a;
output reg out;
output reg [1:0] state;

```

```

always @(posedge clk, negedge reset)
begin
  if(!reset)
    state<=s0;
  else
    begin
      case(state)
        s0:if(!a)
          state<=s0;
        else
          state<=s1;
        s1:if(!a)
          state<=s1;
        else
          state<=s2;
        s2:if(!a)
          state<=s1;
        else
          state<=s2;
      endcase
    end
end
always @(state)
begin
  case(state)

```

```
s0: out<=0;
s1: out<=1;
s2: out<=0;
endcase
end
endmodule
```

Test Bench:

```
module test_moore_machine_2_complement();
reg clk ,reset;
reg a;
wire out;
wire [1:0] state;
moore_machine mo(clk, reset, a, out, state);
always #5 clk = ~clk;
initial begin
    clk = 0;
    reset = 0;
    a = 1;
    #10 reset = 1;
    #10 a = 0;
    #10 a = 1;
    #10 a = 1;
    #10 a = 0;
    #10 a = 1;
    #10 a = 0;
end
initial #80 $finish;
endmodule
```

Waveform:

