


# LAB REPORT-B20EE016

Digital Design - EEL2020

Dhruv

B20EE016

## BCD-Adder

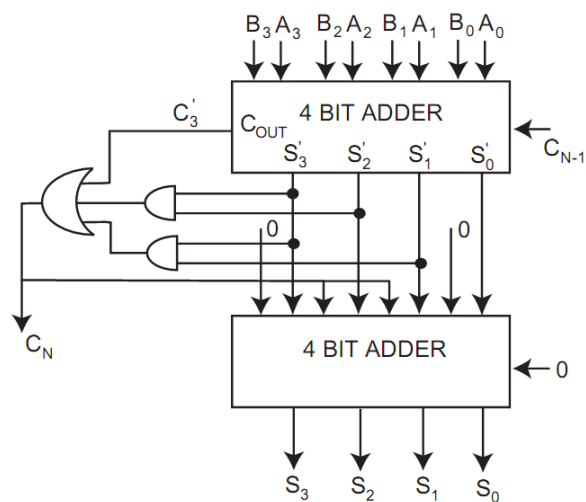

Binary Sum					BCD Sum					Decimal
K	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
.	.	.	.	.	.	.	.	.	.	.
.	.	.	.	.	.	.	.	.	.	.
.	.	.	.	.	.	.	.	.	.	.
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
10 to 19 Binary and BCD codes are not the same										
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

## Code

```

`timescale 1ns / 1ps
module Half_Adder(a,b,sum,carry );
    input a,b;
    output sum ,carry;
    assign sum=a^b;
    assign carry=a&b;
endmodule

module Full_Adder(a,b,c,sum,carry);
    input a,b,c;
    output sum,carry;
    wire sum1,carry1,carry2;

```

```

    Half_Adder H1(b,c,sum1,carry1);
    Half_Adder H2(a,sum1,sum,carry2);
    assign carry=carry1|carry2;
endmodule

module SevenSegmentDisplay(Hex, Led);
    input [0:3] Hex;
    output reg [1:7] Led;
    always@(Hex)
        begin
            case(Hex)
                0 : Led = 7'b1111110;
                1 : Led = 7'b0110000;
                2 : Led = 7'b1101101;
                3 : Led = 7'b1111001;
                4 : Led = 7'b0110011;
                5 : Led = 7'b1011011;
                6 : Led = 7'b1011111;
                7 : Led = 7'b1110000;
                8 : Led = 7'b1111111;
                9 : Led = 7'b1111011;
                default: Led = 7'b0000000;
            endcase
        end
endmodule

module FourBitAdder(
    input [3:0] A,
    input [3:0] B,
    input Cin,
    output [3:0] Sum,
    output Cout
);
    wire [3:0] carry;

    assign carry[0]=Cin;
    Full_Adder F1(A[0],B[0],carry[0],Sum[0],carry[1]);
    Full_Adder F2(A[1],B[1],carry[1],Sum[1],carry[2]);
    Full_Adder F3(A[2],B[2],carry[2],Sum[2],carry[3]);
    Full_Adder F4(A[3],B[3],carry[3],Sum[3],Cout);
    // SevenSegmentDisplay s1(Sum, led);
endmodule

module BCDAdder(
    input [3:0] A,
    input [3:0] B,
    input Cin,
    output [3:0] Sum,
    output Cout,

```

```


    output [6:0] led
);
    reg [3:0] SixOrZero;
    wire temp1,temp2,temp3,temp4,temp5;
    wire [3:0] sum1 ;
    FourBitAdder F11(A,B,Cin,sum1,temp1);
    assign temp2=sum1[3]&sum1[2];
    assign temp3=sum1[3]&sum1[1];
    assign temp4=temp1|temp2|temp3;
    assign Cout=temp4;
    always @(temp4)
    begin
        if (temp4==1) SixOrZero=4'b0110;
        else SixOrZero=4'b0000;
    end
    end
    FourBitAdder F12(sum1,SixOrZero,0,Sum,temp5);

    SevenSegmentDisplay s1(Sum,led);

endmodule

```

## Simulation

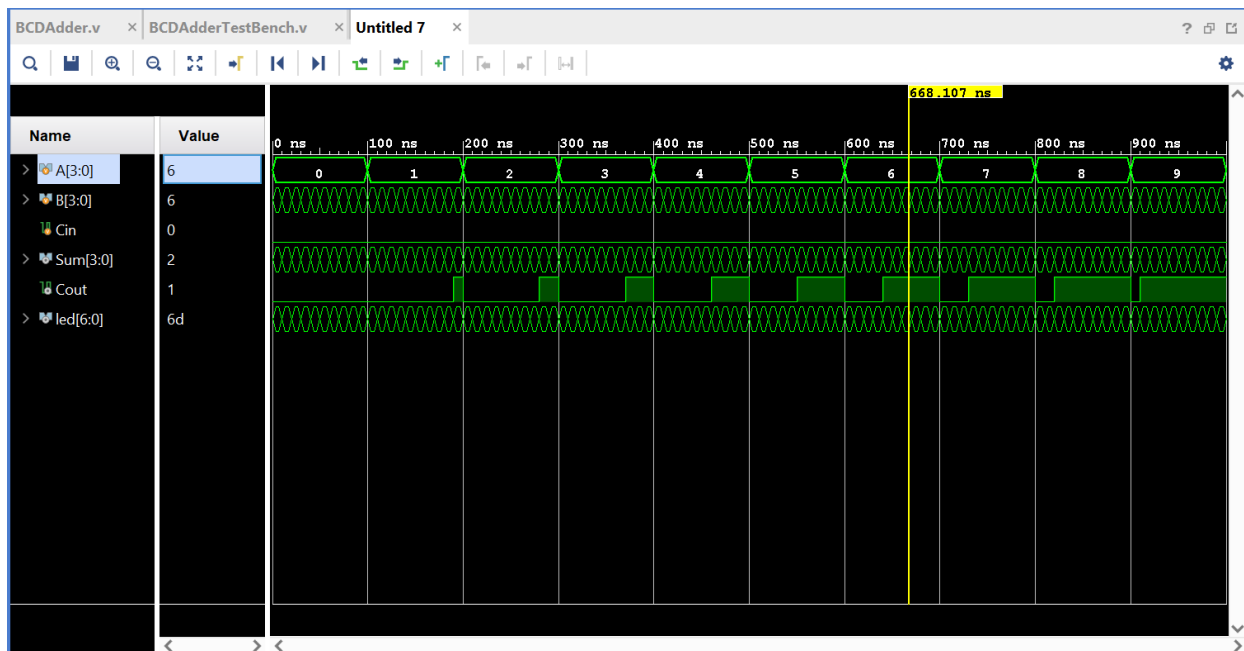

# TestBench


```
`timescale 1ns / 1ps
module BCDAdderTestBench();
    reg[3:0]A,B;
    reg Cin;
    wire [3:0]Sum;
    wire Cout;
    wire [6:0] led;
    integer i,j;

    BCDAdder B11(A,B,Cin,Sum,Cout, led);
    initial

    begin
        A = 0;
        B = 0;
        Cin=1'b0;
        //      A=4'b0000;B=4'b0000;
        //      #10 A=4'b0000;B=4'b0000;
        //      #10 A=4'b0001;B=4'b0101;
        //      #10 A=4'b1000;B=4'b1000;
        for(i=0;i<10;i=i+1) begin
            for(j=0;j<10;j=j+1) begin
                A = i;
                B = j;
                #10;
            end end
        end
    //initial # $finish;

endmodule
```

## BCD-Multiplier

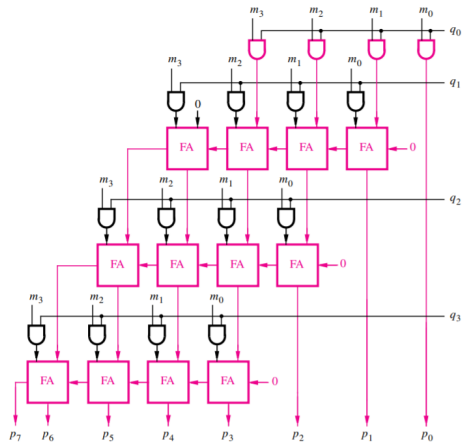

## Code

```
`timescale 1ns / 1ps

module Half_Adder(a,b,sum,carry );
    input a,b;
    output sum ,carry;
    assign sum=a^b;
    assign carry=a&b;
endmodule

module Full_Adder(a,b,c,sum,carry);
    input a,b,c;
    output sum,carry;
    wire sum1,carry1,carry2;
    Half_Adder H1(b,c,sum1,carry1);
    Half_Adder H2(a,sum1,sum,carry2);
    assign carry=carry1|carry2;
endmodule

module SevenSegmentDisplay(Hex,Led);
    input [0:3] Hex;
    output reg [1:7] Led;
    always@(Hex)
    begin
        case(Hex)
            0 : Led = 7'b1111110;
            1 : Led = 7'b0110000;
```

```

        2 : Led = 7'b1101101;
        3 : Led = 7'b1111001;
        4 : Led = 7'b0110011;
        5 : Led = 7'b1011011;
        6 : Led = 7'b1011111;
        7 : Led = 7'b1110000;
        8 : Led = 7'b1111111;
        9 : Led = 7'b1111011;
        default: Led = 7'b0000000;
    endcase
end
endmodule

```

```

module FourBitAdder(
    input [3:0] A,
    input [3:0] B,
    input Cin,
    output [3:0] Sum,
    output Cout
);
    wire [3:0] carry;

    assign carry[0]=Cin;
    Full_Adder F1(A[0],B[0],carry[0],Sum[0],carry[1]);
    Full_Adder F2(A[1],B[1],carry[1],Sum[1],carry[2]);
    Full_Adder F3(A[2],B[2],carry[2],Sum[2],carry[3]);
    Full_Adder F4(A[3],B[3],carry[3],Sum[3],Cout);
    // SevenSegmentDisplay s1(Sum,led);
endmodule

```

```

module bcd_conv(
    input [5:0] Product,
    output reg [3:0] Tens,Ones);
    wire [3:0] k;
    wire [5:0] c;
    wire [3:0] temp;

    always @(Product)
        begin
            if ((Product <= 6'b001001 )==1) begin
                assign Tens=4'b0000;
            end
            else if ((Product >= 6'b001010 & Product < 6'b010100)==1) begin
                assign Tens=4'b0001;
            end
            else if ((Product >= 6'b010100& Product < 6'b011110)==1) begin
                assign Tens=4'b0010;
            end
        end
    end

```

```

        else if ((Product >= 6'b011110 & Product < 6'b101000)==1) begin
            assign Tens=4'b0011;
        end
        else if ((Product >= 6'b101000 & Product < 6'b110010)==1) begin
            assign Tens=4'b0100;
        end
        assign Ones=Product%10;

    end

endmodule

```

```

module BCDMultiplier(
    input [2:0] A,B,
    output[5:0] Product,
    output [6:0] LedTens,
    output [6:0] LedOnes,
    output[3:0] Ones,
    output[3:0] Tens
);

    wire[3:0] FirstProduct;
    assign FirstProduct[0]=A[0]&B[0];
    assign FirstProduct[1]=A[1]&B[0];
    assign FirstProduct[2]=A[2]&B[0];
    assign FirstProduct[3]=0;

    wire[3:0] SecondProduct;
    assign SecondProduct[0]=0;
    assign SecondProduct[1]=A[0]&B[1];
    assign SecondProduct[2]=A[1]&B[1];
    assign SecondProduct[3]=A[2]&B[1];

    wire [3:0] FirstSum;
    wire FirstCarry;
    FourBitAdder F1(FirstProduct,SecondProduct,0,FirstSum,FirstCarry);

    wire[3:0] FirstProduct2;
    assign FirstProduct2[0]=FirstSum[1];
    assign FirstProduct2[1]=FirstSum[2];
    assign FirstProduct2[2]=FirstSum[3];
    assign FirstProduct2[3]=FirstCarry;

    wire[3:0] SecondProduct2;
    assign SecondProduct2[0]=0;
    assign SecondProduct2[1]=A[0]&B[2];
    assign SecondProduct2[2]=A[1]&B[2];
    assign SecondProduct2[3]=A[2]&B[2];

```

```


wire [3:0] FirstSum2;
wire FirstCarry2;
FourBitAdder F2(FirstProduct2,SecondProduct2,0,FirstSum2,FirstCarry2);

assign Product[0]=FirstSum[0];
assign Product[1]=FirstSum2[0];
assign Product[2]=FirstSum2[1];
assign Product[3]=FirstSum2[2];
assign Product[4]=FirstSum2[3];
assign Product[5]=FirstCarry2;

//wire [3:0] Tens,Ones;
bcd_conv cnv(Product,Tens,Ones);
SevenSegmentDisplay s1(Tens,LedTens);
SevenSegmentDisplay s2(Ones,LedOnes);
endmodule

```

## Simulation

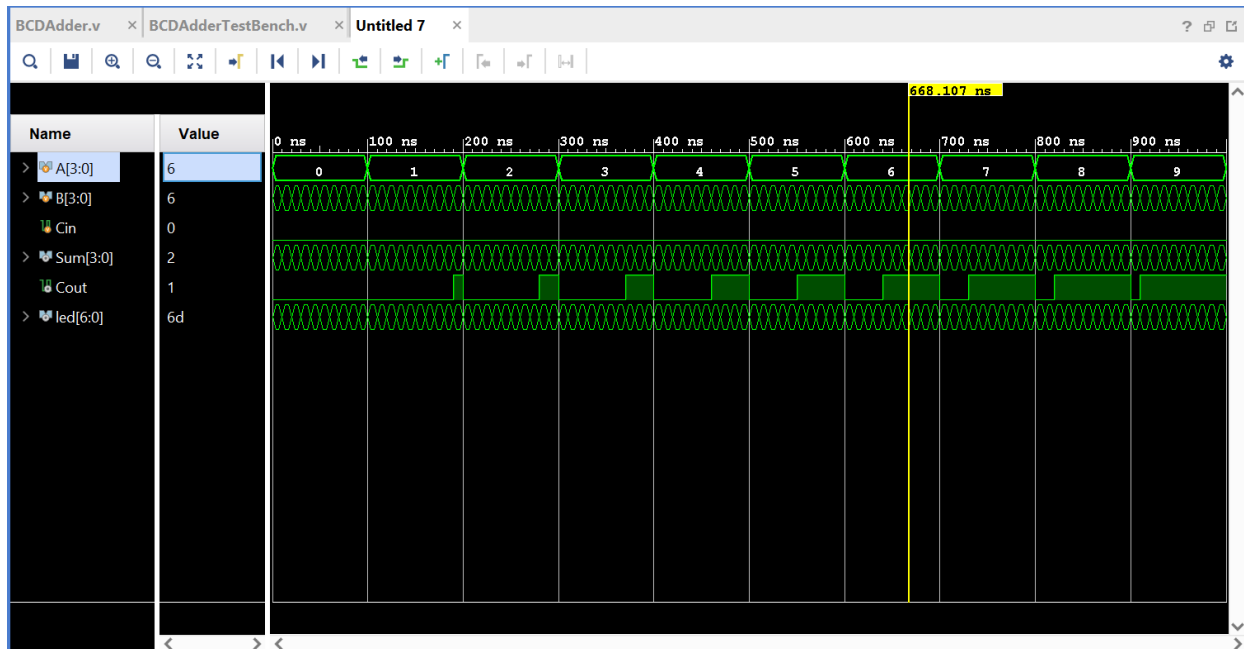

## TestBench

```

`timescale 1ns / 1ps
module BCDMultiplierTestBench();
    reg [2:0] A,B;

```



```

wire [5:0] Product;
wire [6:0] LedOnes;
wire [6:0] LedTens;
wire [3:0] Ones;
wire [3:0] Tens;
integer i, j;
BCDMultiplier M1(A,B,Product,LedOnes,LedTens,Ones,Tens);
initial
begin
for(i = 0; i<=7 ; i=i+1)begin
for(j = 0 ; j<=7 ; j=j+1)begin
A = i;
B = j;
#10;
end
end
end
initial #800 $finish;
endmodule

```

## BCD-Subtractor

### Code

```

`timescale 1ns / 1ps
module TensComplement(A,complement);
input [3:0] A;
output [3:0] complement;
assign complement[0] = A[0];
assign complement[1] = A[1]&A[0]|A[3]&(~A[0])|A[2]&(~A[1])&(~A[0]);
assign complement[2] = A[2]&(~A[1])|A[2]&(~A[0])|(~A[2])&A[1]&A[0];
assign complement[3] = (~A[2])&A[1]&(~A[0])|(~A[3])&(~A[2])&(~A[1])&A[0];
endmodule

module SevenSegmentDisplay(Hex,Led);
input [0:3] Hex;
output reg [1:7] Led;
always@(Hex)
begin
case(Hex)
0 : Led = 7'b1111110;
1 : Led = 7'b0110000;
2 : Led = 7'b1101101;
3 : Led = 7'b1111001;
4 : Led = 7'b0110011;
5 : Led = 7'b1011011;
6 : Led = 7'b1011111;

```

```

        7 : Led  = 7'b1110000;
        8 : Led  = 7'b1111111;
        9 : Led  = 7'b1111011;
        default: Led = 7'b0000000;
    endcase
end
endmodule


module BCDSubtractor(
    input [3:0] A,
    input [3:0] B,
    input Cin,
    output reg [3:0] Sum,
    output reg SignPositive
);
wire temp4;
wire [3:0] Output,NB,NSum;
wire [6:0] temp4led;

TensComplement A1(B,NB);
BCDAdder BCD1(A,NB,Cin,Output,temp4,temp4led);
TensComplement A22(Output,NSum);
always @(temp4)
    begin
        if (temp4==1) begin
            SignPositive=1'b1;
            assign Sum=Output;
        end
        else begin
            assign SignPositive=1'b0;
            assign Sum=NSum;
        end
    end
end

endmodule

```

## Simulation

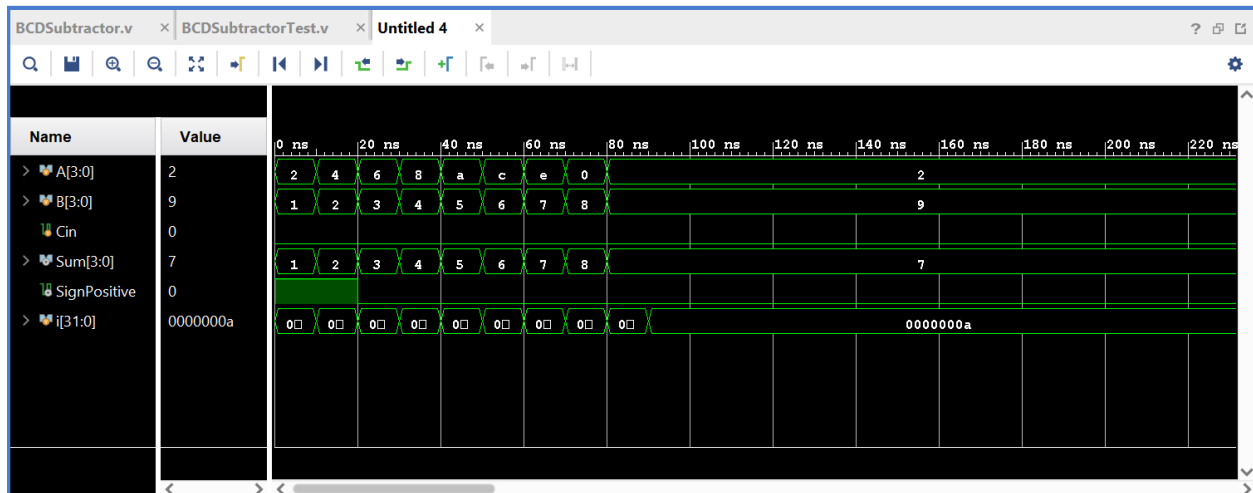

;

## TestBench

```
`timescale 1ns / 1ps
module BCDSubtractorTest();
    reg[3:0]A,B;
    reg Cin;
    wire [3:0]Sum;
    wire SignPositive;
    integer i;
    BCDSubtractor B11(A,B,Cin,Sum,SignPositive);
    initial
    begin

        for (i = 1; i<10;i=i+1)begin
            A=2*i;
            B=i;
            Cin=0;
            #10;
        end
    end

endmodule
```

## CONCLUSION

- In Bcd Adder we take 4bit numbers hence we can represnt only 0-15 numbers but on 7 segment display we can display 0-9 only so when our answer after addition

comes out to be greater than 9 we add 6 to it which in turn make us skip 10-15 numbers (including 10-15) which in order helps to display it on two 7 segment display

- In order to calculate the BCD subtraction we take 10s complement of the number